

## Alexander & Sadiku Example Problem 10.6

Michael Gustafson

> restart

### Handy functions for dealing with phasors

>  $j := I$

$$j := I \quad (1)$$

>  $polard := (mag, angd) \rightarrow \text{polar}(mag, angd * \pi / 180)$

$$\text{polard} := (\text{mag}, \text{angd}) \rightarrow \text{polar}\left(\text{mag}, \frac{1}{180} \text{angd} \pi\right) \quad (2)$$

>  $argumentd := (\text{num}) \rightarrow \text{argument}(\text{num}) * 180 / \pi$

$$\text{argumentd} := \text{num} \rightarrow \frac{180 \text{argument}(\text{num})}{\pi} \quad (3)$$

```
> listphasors := proc(plist) local k
for k from 1 to nops(plist[ ]) do
printf("%s = %f < %f deg\n", lhs(plist[ ][k]), evalf(abs(rhs(plist[ ][k]))),
evalf(argumentd(rhs(plist[ ][k]))))
end do end proc:
```

### Circuit equations

>  $KCLn2 := \frac{(Vn2 - Va)}{j \cdot \text{omega} \cdot L} - Ib + \frac{Vo}{R1} = 0$

$$KCLn2 := -\frac{I(Vn2 - Va)}{\omega L} - Ib + \frac{Vo}{R1} = 0 \quad (4)$$

>  $KCLn3 := -\frac{Vo}{R1} + j \cdot \text{omega} \cdot C \cdot (Vn2 - Vo) + \frac{(Vn2 - Vo - Vc)}{R2} = 0$

$$KCLn3 := -\frac{Vo}{R1} + I \omega C (Vn2 - Vo) + \frac{Vn2 - Vo - Vc}{R2} = 0 \quad (5)$$

### Solve circuit equations

>  $MySoln := \text{solve}(\{KCLn2, KCLn3\}, [Vn2, Vo])$

$$\text{MySoln} := \left[ \begin{aligned} Vn2 = & - \left( I (\omega L Vc - I Va R2 + \omega C R1 R2 Va - I R1 Va + Ib \omega L R2 \right. \\ & \left. + I \omega^2 C R1 R2 Ib L + Ib \omega L R1) \right) / (-I \omega L + \omega^2 L C R2 - R2 - I \omega C R1 R2 \right. \end{aligned} \right] \quad (6)$$

$$- R1), \quad Vo = \frac{R1 (Vc - Va - I Ib \omega L - I \omega C R2 Va + \omega^2 C R2 Ib L)}{-I \omega L + \omega^2 L C R2 - R2 - I \omega C R1 R2 - R1} \quad (6)$$

### Define lists for each frequency independently

>  $Valsa := R1 = 1, R2 = 4, L = 2, C = 0.1, \text{omega} = 2, Va = \text{polard}(10, 0), Ib = 0, Vc = 0$   
 $Valsa := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 2, Va = \text{polar}(10, 0), Ib = 0, Vc = 0$       (7)

>  $Valsb := R1 = 1, R2 = 4, L = 2, C = 0.1, \text{omega} = 5, Va = 0, Ib = \text{polard}(2, -90), Vc = 0$

$$Valsb := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 5, Va = 0, Ib = \text{polar}\left(2, -\frac{1}{2} \pi\right), Vc = 0 \quad (8)$$

>  $Valsc := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 0, Va = 0, Ib = 0, Vc = polar(5, 0)$   
 $Valsc := R1 = 1, R2 = 4, L = 2, C = 0.1, \omega = 0, Va = 0, Ib = 0, Vc = polar(5, 0)$  (9)

### Find solutions for each frequency

>  $MySolna := subs(Vals, MySoln)$   
 $MySolna := [[Vn2 = (0.1826484018 + 0.06849315068 I) (-5 I polar(10, 0)$  (10)  
 $+ 0.8 polar(10, 0)), Vo = (-0.06849315068 + 0.1826484018 I) (-polar(10,$

$0) - 0.8 I polar(10, 0))]]$

>  $MySolnb := subs(Valsb, MySoln)$

$MySolnb := [[Vn2 = (0.03252032520 - 0.04065040650 I) \left( 50 \text{ polar}\left(2, -\frac{1}{2} \pi\right) + 20.0 I \text{ polar}\left(2, -\frac{1}{2} \pi\right) \right), Vo = (0.04065040650 + 0.03252032520 I) \left( -10 I \text{ polar}\left(2, -\frac{1}{2} \pi\right) + 20.0 \text{ polar}\left(2, -\frac{1}{2} \pi\right) \right)]]$  (11)

>  $MySolnc := subs(Valsc, MySoln)$

$MySolnc := [[Vn2 = 0. - 0.1 I, Vo = (-0.2000000000 + 0.1 I) polar(5, 0)]]$  (12)

### Find phasors for each frequency

>  $listphasors(MySolna)$

$Vn2 = 9.877484 < -60.353678 \text{ deg}$

$Vo = 2.498097 < -30.784147 \text{ deg}$

>  $listphasors(MySolnb)$

$Vn2 = 5.606810 < -119.538782 \text{ deg}$

$Vo = 2.328101 < -77.905243 \text{ deg}$

>  $listphasors(MySolnc)$

$Vn2 = 0.000000 < \text{NaN deg}$

$Vo = 1.000000 < 180.000000 \text{ deg}$

**Conclusion:**  $vo(t) = 2.498 \cos(2 t - 30.78 \text{ deg}) + 2.328 \cos(5 t - 77.91 \text{ deg}) - 1$